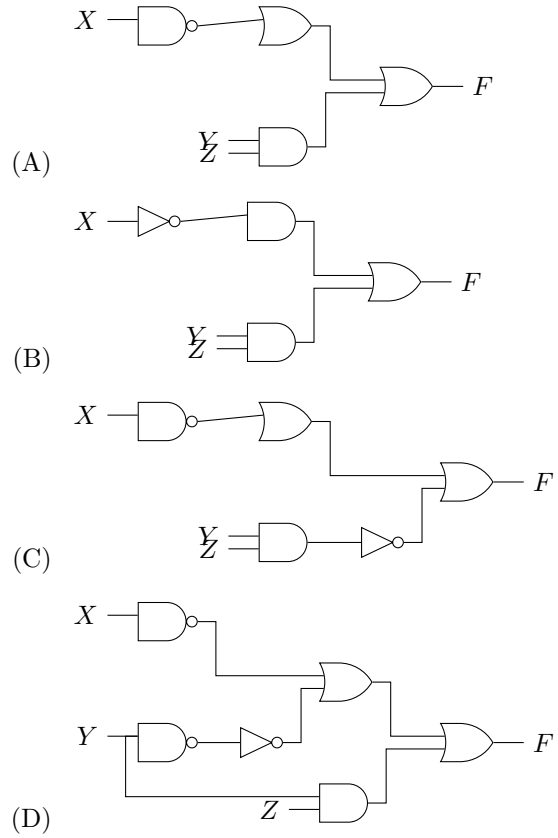


GATE Electrical Engineering (EE)

Given that the function $F = XY + YZ$ **Q.53** Which of the following circuits is a realization of the above function F ?



Answer: The circuit that realizes the function $F = XY + YZ$ is option (B).